

Seat No.	
----------	--

**T.E.(Electronics and TelecommunicationEngineering)  
(Semester -VI)(Old)Examination, April - 2016  
VLSI Design  
Sub. Code: 45694**

Day and Date : Thursday, 21 - 04 - 2016  
Time :03.00 p.m. to 6.00 p.m.

Total Marks :100

- Instructions :
- 1) All questions are compulsory.
  - 2) Numbers to the right indicates full marks.
  - 3) Assume suitable data wherever necessary.

**SECTION-I**

**Q1) Solve any three:-** **[18]**

- a) Which are the different types of 'Operators' that operate on signals, variables and constants in VHDL? Summarize all types and with suitable examples, elaborate 'Logical' operators.
- b) Write a VHDL code for 3:8 decoder using 'Case' statement.
- c) With suitable examples of each class, briefly write about various classes of data types used in VHDL programming.
- d) Differentiate MOORE and MELAY machines with suitable examples.

**Q2) Solve any two:-** **[16]**

- a) With neat and suitable block diagram, briefly explain VLSI design flow.
- b) Write a VHDL code for 4:1, 8 bit wide multiplexer using behavioral, and data flow type of modeling.
- c) What is meant by 'clock skew' and 'clock jitter'? Briefly write about these concepts with suitable examples.

**P.T.O.**

**Q3) Solve any two:**

**[16]**

- a) Explain briefly the different levels of abstraction.
- b) Write a VHDL code for 4 bit Johnson counter using structural type of modeling.
- c) Write a VHDL code for BCD to 7-segment(common anode type)decoder.

**SECTION-II**

**Q4) Solve any three:**

**[18]**

- a) Which are the different types of 'Attributes' to which VHDL supports? Elaborate 'Array' type of attributes with proper syntax and its function.
- b) What is the role of simulators in VHDL code testing? Elaborate cycle based simulator with suitable example.
- c) Explain 'inertial' and 'transport' delay used in VHDL programming with suitable examples. Draw the respective timing diagrams also.
- d) Write a VHDL code for 'D' flip flop with 2-to-1 multiplexer at the 'D' input using WAIT statement.

**Q5) Solve any two:**

**[16]**

- a) Draw and explain complete block diagram of data path section of general purpose microprocessor EC-2.
- b) With the help of neat sketch diagram explain XC9572 input/output block which interfaces internal logic with I/O pins.
- c) Explain briefly with suitable example Built In Self Testing(BIST) technique used in testing digital ICs.

Q6) Solve any two:-

[16]

- a) Briefly write about s-a-1(stuck-at-1) and s-a-0(stuck-at-0)model faults with suitable examples used while testing combinational logic.
- b) Explain the concept of look-up table used in CLB of Spartan-II FPGA. Draw necessary sketches of LUT and CLB.
- c) Draw the complete block diagram of EC-2 general purpose microprocessor. Briefly write about the various instructions derived for the same.

