

Seat No.	
----------	--

**SJ - 786**

Total No. of Pages : 2

**T.E. (Electronics & Telecommunication) (Part - I) (Semester - V)**  
**Examination, November - 2016**

**POWER ELECTRONICS (Revised)**

**Sub. Code : 66317**

**Day and Date : Thursday, 24 - 11 - 2016**

**Total Marks : 100**

**Time : 02.30 p.m. to 05.30 p.m.**

- Instruction :**
- 1) All questions are compulsory.
  - 2) Figures to the right indicates full marks.
  - 3) Assume suitable data if necessary.

**SECTION - I**

**Q1) Solve any two :**

**[16]**

- a) Draw and explain construction & V-I characteristics of SCR.
- b) Explain  $dv/dt$  and  $di/dt$  protection circuits for SCR.
- c) Explain necessity and ratings of SCR in series & parallel connections of SCR with circuit diagram.

**Q2) Solve any two :**

**[16]**

- a) With the help of circuit diagram & waveform explain single phase fullwave controlled rectifier with inductive load.
- b) Mention different turn on method of SCR. Explain PVT triggering circuit with waveforms.
- c) The single phase half-wave controlled rectifier is connected to 230V, 50Hz supply. If delay angle is  $45^\circ$  find out.
  - i)  $V_{dc}$
  - ii)  $V_{rms}$
  - iii) Harmonic factor
  - iv) Displacement factor

**P.T.O.**

**Q3)** Write notes on any three.

- a) Power ratings of SCR.
- b) Class-A commutation of SCR.
- c) GTO
- d) Effect of free wheeling diode

**SECTION - II**

**Q4)** Solve any two :

**[16]**

- a) Explain with help of circuit diagram & waveforms single phase bridge inverter.
- b) With the help of circuit diagram & waveforms, explain morgan's chopper.
- c) Explain output voltage control techniques of inverter.

**Q5)** Solve any two :

**[16]**

- a) Explain principle of operation of dielectric heating and its applications.
- b) Explain with circuit diagram & waveforms three phase bridge inverter.
- c) Explain with circuit diagram speed control of DC series motor using chopper.

**Q6)** Writes notes on any three :

**[18]**

- a) PLC-Architecture & Applications
- b) SMPS
- c) Static circuit breakers
- d) SCADA-Architecture & Applications

